#### 1次近似(1)

$$f(v_{1}, v_{2}, I_{S}, K) = \frac{I_{S}}{2} \left( 1 + \sqrt{\frac{2K}{I_{S}}} (v_{1} - v_{2}) \sqrt{1 - \frac{K}{2I_{S}}} (v_{1} - v_{2})^{2} \right)$$

$$\approx \frac{I_{S}}{2} \left( 1 + \sqrt{\frac{2K}{I_{S}}} (v_{1} - v_{2}) \right)$$

$$I_{d1} = f(v_{CTI})$$

$$\approx \frac{I_{dB1}}{2} \left( \frac{I_{dB1}}{2} \right)$$

$$I_{\text{dB}} = f(v_{\text{in}}, -v_{\text{in}}, I_{\text{C}}, K_{\text{B}})$$

$$\approx \frac{I_{\text{C}}}{2} \left( 1 + 2 \sqrt{\frac{2K_{\text{B}}}{I_{\text{C}}}} v_{\text{in}} \right)$$

$$I_{\text{dB}} = f(-v_{\text{in}}, v_{\text{in}}, I_{\text{C}}, K_{\text{B}})$$

$$\cong \frac{I_{\text{C}}}{2} \left(1 - 2\sqrt{\frac{2K_{\text{B}}}{I_{\text{C}}}}v_{\text{in}}\right)$$

$$I_{d1} = f(v_{\text{CTRL}}, -v_{\text{CTRL}}, I_{\text{dB1}}, K_{\text{A}})$$

$$\cong \frac{I_{\text{dB1}}}{2} \left( 1 + 2 \sqrt{\frac{2K_{\text{A}}}{I_{\text{dB1}}}} v_{\text{CTRL}} \right)$$

$$\cong \frac{I_{\text{C}}}{4} \left( 1 + 2 \sqrt{\frac{2K_{\text{B}}}{I_{\text{C}}}} v_{\text{in}} \right) \left( 1 + 2 \sqrt{\frac{2K_{\text{A}}}{I_{\text{C}}}} \left( 1 - \sqrt{\frac{2K_{\text{B}}}{I_{\text{C}}}} v_{\text{in}} \right) v_{\text{CTRL}} \right)$$

$$= \frac{I_{\text{C}}}{4} \left( 1 + 2 \sqrt{\frac{2K_{\text{B}}}{I_{\text{C}}}} v_{\text{in}} \right) \left( 1 + 4 \sqrt{\frac{K_{\text{A}}}{I_{\text{C}}}} v_{\text{CTRL}} - 4\sqrt{2} \frac{\sqrt{K_{\text{A}}K_{\text{B}}}}{I_{\text{C}}} v_{\text{in}} v_{\text{CTRL}} \right)$$

$$\cong \frac{I_{\text{C}}}{4} \left( 1 + 2 \sqrt{\frac{2K_{\text{B}}}{I_{\text{C}}}} v_{\text{in}} + 4 \sqrt{\frac{K_{\text{A}}}{I_{\text{C}}}} v_{\text{CTRL}} + 4\sqrt{2} \frac{\sqrt{K_{\text{A}}K_{\text{B}}}}{I_{\text{C}}} v_{\text{in}} v_{\text{CTRL}} \right)$$

#### 1次近似(2)

$$I_{d1} = f(v_{\text{CTRL}}, -v_{\text{CTRL}}, I_{\text{dB1}}, K_{\text{A}})$$

$$\cong \frac{I_{\mathrm{C}}}{4} \left( 1 + 2 \sqrt{\frac{2K_{\mathrm{B}}}{I_{\mathrm{C}}}} v_{\mathrm{in}} + 4 \sqrt{\frac{K_{\mathrm{A}}}{I_{\mathrm{C}}}} v_{\mathrm{CTRL}} + 4\sqrt{2} \frac{\sqrt{K_{\mathrm{A}}K_{\mathrm{B}}}}{I_{\mathrm{C}}} v_{\mathrm{in}} v_{\mathrm{CTRL}} \right)$$

 $I_{d2} = f(-v_{\text{CTRL}}, v_{\text{CTRL}}, I_{\text{dB1}}, K_{\text{A}})$ 

$$\cong \frac{I_{\mathrm{C}}}{4} \left( 1 + 2 \sqrt{\frac{2K_{\mathrm{B}}}{I_{\mathrm{C}}}} v_{\mathrm{in}} - 4 \sqrt{\frac{K_{\mathrm{A}}}{I_{\mathrm{C}}}} v_{\mathrm{CTRL}} - 4\sqrt{2} \frac{\sqrt{K_{\mathrm{A}}K_{\mathrm{B}}}}{I_{\mathrm{C}}} v_{\mathrm{in}} v_{\mathrm{CTRL}} \right)$$

 $I_{d3} = f(-v_{\text{CTRL}}, v_{\text{CTRL}}, I_{\text{dB2}}, K_{\text{A}})$ 

$$\cong \frac{I_{\mathrm{C}}}{4} \left( 1 - 2 \sqrt{\frac{2K_{\mathrm{B}}}{I_{\mathrm{C}}}} v_{\mathrm{in}} - 4 \sqrt{\frac{K_{\mathrm{A}}}{I_{\mathrm{C}}}} v_{\mathrm{CTRL}} + 4\sqrt{2} \frac{\sqrt{K_{\mathrm{A}}K_{\mathrm{B}}}}{I_{\mathrm{C}}} v_{\mathrm{in}} v_{\mathrm{CTRL}} \right)$$

 $I_{d4} = f(v_{\text{CTRL}}, -v_{\text{CTRL}}, I_{\text{dB2}}, K_{\text{A}})$ 

$$\cong \frac{I_{\mathrm{C}}}{4} \left( 1 - 2 \sqrt{\frac{2K_{\mathrm{B}}}{I_{\mathrm{C}}}} v_{\mathrm{in}} + 4 \sqrt{\frac{K_{\mathrm{A}}}{I_{\mathrm{C}}}} v_{\mathrm{CTRL}} - 4\sqrt{2} \frac{\sqrt{K_{\mathrm{A}}K_{\mathrm{B}}}}{I_{\mathrm{C}}} v_{\mathrm{in}} v_{\mathrm{CTRL}} \right)$$

 $V_{\text{out}} = R_{\text{L}}(I_{\text{d1}} - I_{\text{d2}} + I_{\text{d3}} - I_{\text{d4}})$  $\approx 4\sqrt{2}\sqrt{K_{\text{A}}K_{\text{B}}}R_{\text{L}}v_{\text{in}}v_{\text{CTRL}}$ 

小信号等価回路を利用した結果と (当然ながら)一致

#### 飽和領域でのプロット~準備~

$$\left(I_{\rm C} = 1000 \,\mu\text{A}, \qquad 2K_{\rm A} = K_{\rm B} = 500 \,\mu\text{S/V}, \qquad R_{\rm L} = 400 \,\Omega, \qquad g(x) = x\sqrt{1-\left(\frac{x}{2}\right)^2}, \qquad h(x) = 1+g(x)\right)$$

$$\begin{split} f(v_1, v_2, I_{\text{C}}, K_{\text{B}}) &= \frac{I_{\text{C}}}{2} \left( 1 + \sqrt{\frac{2K_{\text{B}}}{I_{\text{C}}}} (v_1 - v_2) \sqrt{1 - \frac{K_{\text{B}}}{2I_{\text{C}}}} (v_1 - v_2)^2 \right) \\ &= 500 \ \mu\text{A} \left( 1 + (v_1 - v_2) \sqrt{1 - \left(\frac{v_1 - v_2}{2}\right)^2} \right) \\ &= 500 \ \mu\text{A} \cdot h(v_1 - v_2) \\ f(v_3, v_4, I_{\text{dB1}}, K_{\text{A}}) &= \frac{I_{\text{dB1}}}{2} \left( 1 + \sqrt{\frac{2K_{\text{A}}}{I_{\text{dB1}}}} (v_3 - v_4) \sqrt{1 - \frac{K_{\text{A}}}{2I_{\text{dB1}}}} (v_3 - v_4)^2} \right) \\ &= 250 \ \mu\text{A} \cdot h(v_1 - v_2) \left( 1 + \frac{v_3 - v_4}{\sqrt{h(v_1 - v_2)}} \sqrt{1 - \left(\frac{v_3 - v_4}{2\sqrt{h(v_1 - v_2)}}\right)^2} \right) \\ &= 250 \ \mu\text{A} \cdot h(v_1 - v_2) \cdot h\left(\frac{v_3 - v_4}{\sqrt{h(v_1 - v_2)}}\right) \end{split}$$

$$I_{\text{dB1}} = f(v_{\text{in}}, -v_{\text{in}}, I_{\text{C}}, K_{\text{B}}) = 500 \, \mu\text{A} \cdot g(2v_{\text{in}})$$

$$I_{\text{dB2}} = f(-v_{\text{in}}, v_{\text{in}}, I_{\text{C}}, K_{\text{B}}) = 500 \, \mu\text{A} \cdot g(-2v_{\text{in}})$$

$$I_{\text{d1}} = f(v_{\text{CTRL}}, -v_{\text{CTRL}}, I_{\text{dB1}}, K_{\text{A}})$$

$$= 250 \, \mu\text{A} \cdot h(2v_{\text{in}}) \left[ 1 + g \left( \frac{2v_{\text{CTRL}}}{\sqrt{h(2v_{\text{in}})}} \right) \right]$$

$$I_{\text{d2}} = f(-v_{\text{CTRL}}, v_{\text{CTRL}}, I_{\text{dB1}}, K_{\text{A}})$$

$$= 250 \, \mu\text{A} \cdot h(2v_{\text{in}}) \left[ 1 + g \left( -\frac{2v_{\text{CTRL}}}{\sqrt{h(2v_{\text{in}})}} \right) \right]$$

$$I_{\text{d3}} = f(-v_{\text{CTRL}}, v_{\text{CTRL}}, I_{\text{dB2}}, K_{\text{A}})$$

$$= 250 \, \mu\text{A} \cdot h(-2v_{\text{in}}) \left[ 1 + g \left( -\frac{2v_{\text{CTRL}}}{\sqrt{h(-2v_{\text{in}})}} \right) \right]$$

$$I_{\text{d4}} = f(v_{\text{CTRL}}, -v_{\text{CTRL}}, I_{\text{dB2}}, K_{\text{A}})$$

$$= 250 \, \mu\text{A} \cdot h(-2v_{\text{in}}) \left[ 1 + g \left( -\frac{2v_{\text{CTRL}}}{\sqrt{h(-2v_{\text{in}})}} \right) \right]$$

### 飽和領域でのプロット例~gnuplot~

$$\left(I_{\rm C} = 1000 \,\mu\text{A}, \qquad 2K_{\rm A} = K_{\rm B} = 500 \,\mu\text{S/V}, \qquad R_{\rm L} = 400 \,\Omega, \qquad g(x) = x \sqrt{1 - \left(\frac{x}{2}\right)^2}, \qquad h(x) = 1 + g(x)\right)$$

g(x) が奇関数であることに注意して,

$$(I_{\rm d1} - I_{\rm d2}) + (I_{\rm d3} - I_{\rm d4}) = 250 \,\mu\text{A} \cdot h(2v_{\rm in}) \cdot 2g \left(\frac{2v_{\rm CTRL}}{\sqrt{h(2v_{\rm in})}}\right) + 250 \,\mu\text{A} \cdot h(-2v_{\rm in}) \cdot (-2)g \left(\frac{2v_{\rm CTRL}}{\sqrt{h(-2v_{\rm in})}}\right)$$


$$= 500 \,\mu\text{A} \cdot \left[1 + g(2v_{\rm in})\right] \cdot g \left(\frac{2v_{\rm CTRL}}{\sqrt{1 + g(2v_{\rm in})}}\right) - 500 \,\mu\text{A} \cdot \left[1 - g(2v_{\rm in})\right] \cdot g \left(\frac{2v_{\rm CTRL}}{\sqrt{1 - g(2v_{\rm in})}}\right)$$

$$V_{\rm out} = R_{\rm L}(I_{\rm d1} - I_{\rm d2} + I_{\rm d3} - I_{\rm d4})$$

$$= 0.2 \,\text{V} \cdot \left[\left(1 + g(2v_{\rm in})\right) \cdot g \left(\frac{2v_{\rm CTRL}}{\sqrt{1 + g(2v_{\rm in})}}\right) - \left(1 - g(2v_{\rm in})\right) \cdot g \left(\frac{2v_{\rm CTRL}}{\sqrt{1 - g(2v_{\rm in})}}\right)\right]$$

$$V_{\rm out} \cong 4\sqrt{2}\sqrt{K_{\rm A}K_{\rm B}}R_{\rm L}v_{\rm in}v_{\rm CTRL} = 0.8 \,[\text{V}^{-2}] \cdot v_{\rm in}v_{\rm CTRL}$$

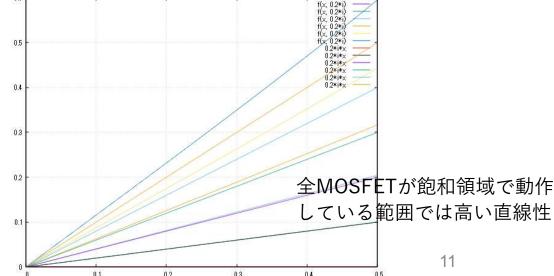g(x)=x\*sqrt(1-(x/2.0)\*\*2) f(x,y)=(1+g(x))\*g(y/sqrt(1+g(x)))-(1-g(x))\*g(y/sqrt(1-g(x)))set xrange [0:0.5] plot for [i=0:5] f(x, 0.2\*i)replot for [i=0:5] 0.2\*i\*x



## プロット例~gnuplot~

 $(I_{\rm C} = 1000 \,\mu\text{A}, \qquad 2K_{\rm A} = K_{\rm B} = 500 \,\mu\text{S/V}, \qquad R_{\rm L} = 400 \,\Omega,)$ 

f(v1, v2, IS, K) = (abs(v1-v2) < sqrt(IS/K) ? (IS/2)\*(1 + sqrt(2\*K/IS)\*(v1-v2)\*sqrt(1 - K/(2\*IS)\*(v1-v2)\*\*2)) : (IS/2)\*(1 + sgn(v1-v2))) Vout(x, y) = RL\*(f(y, -y, f(x, -x, IC, K), K/2) - f(-y, y, f(x, -x, IC, K), K/2) + f(-y, y, f(-x, x, IC, K), K/2) - f(y, -y, f(-x, x, IC, K), K/2)) K = 0.0005


IC = 0.001

RL= 400

set xrange [-1:1]

plot for [i=0:6] Vout(x, 0.2\*i)

replot for [i=0:6] 0.8\*x\*0.2\*i

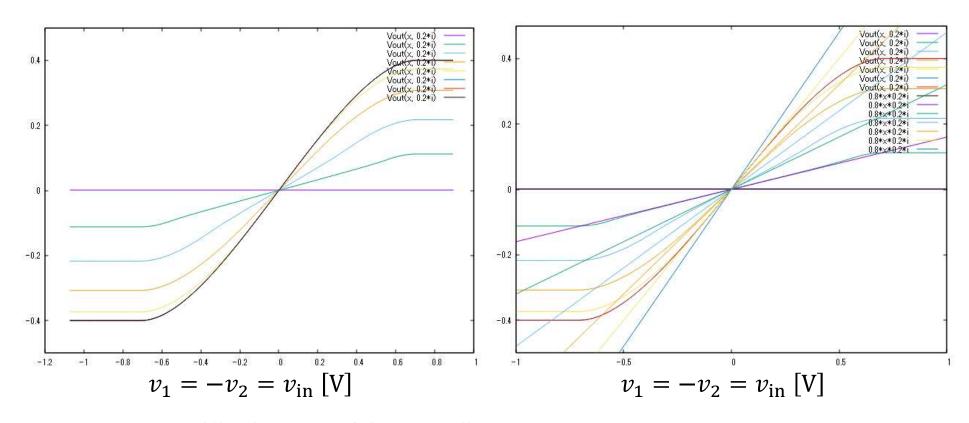

# プロット例~gnuplot~ $(I_{\rm C} = 1000 \, \mu A, 2K_{\rm A} = K_{\rm B} = 500 \, \mu {\rm S/V}, R_{\rm L} = 400 \, \Omega,)$

f(v1, v2, IS, K) = (abs(v1-v2) < sqrt(IS/K)? (IS/2)\*(1 + sqrt(2\*K/IS)\*(v1-v2)\*sqrt(1 - K/(2\*IS)\*(v1-v2)\*\*2)) : (IS/2)\*(1 + sgn(v1-v2))) $Vout(x, y) = RL^*(f(y, -y, f(x, -x, IC, K), K/2) - f(-y, y, f(x, -x, IC, K), K/2) + f(-y, y, f(-x, x, IC, K), K/2) - f(y, -y, f(-x, x, IC, K), K/2))$ K = 0.0005

IC = 0.001

RL= 400

set xrange [-1:1]

plot for [i=0:6] Vout(0.2\*i, x)

replot for [i=0:6] 0.8\*x\*0.2\*i

